

# Power Semiconductors and ICs for Electric-Vehicle Charging

Vladimir SCARPA

Technical Marketing Power, EMEA

[vladimir.scarpa@st.com](mailto:vladimir.scarpa@st.com)




- Electro-vehicle (EV) Charger Introduction
- Main Concept and Topologies
- Practical Example
- Available Development Tools
- Q&A Session

- Electro-vehicle (EV) Charger Introduction
- Main Concept and Topologies
- Practical Example
- Available Development Tools
- Q&A Session

# Charging an Electrical Vehicle

## AC, DC and Wireless Chargers

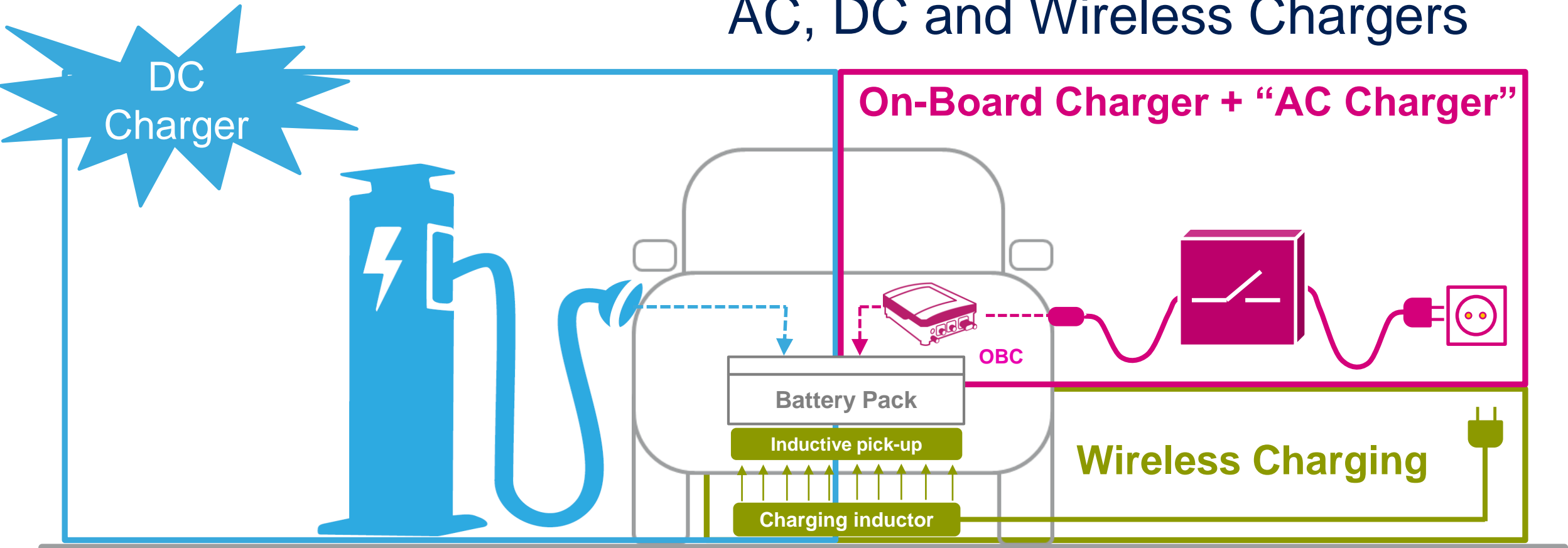


### Advantages of DC Chargers:

- ✓ Charging power not limited to OBC → short charging times.
- ✓ No extra volume and weight inside the car.
- ✓ Does not require same reliability level of OBC → lower cost per kW

# Power of DC Chargers


DC, FC and HPC are CharIn Standards

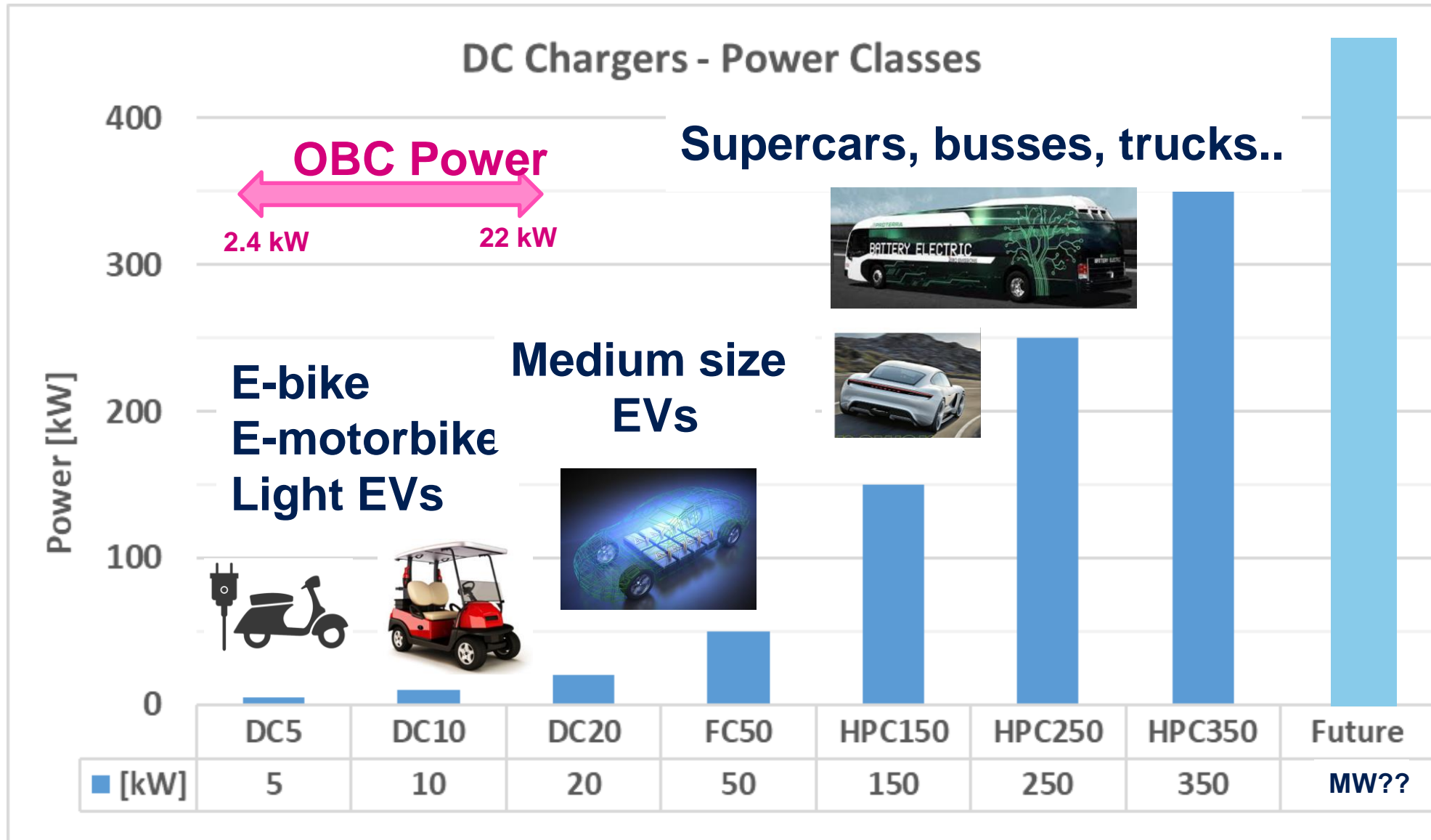

# High Power DC Chargers
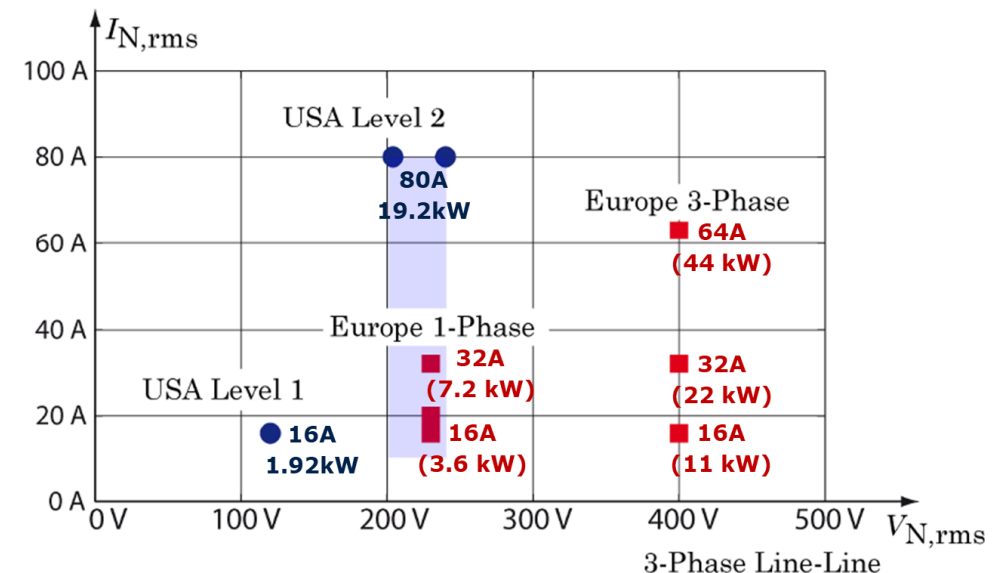
## Technical & Economical Issues

- Grid cables and connectors from **16/32A/64A – 11kW/22kW/44kW** in European grid – are normally **easily accessible**.
- **Above this value**, charger needs to be installed directly to the **transmission line**. This requires a **low frequency transformer**, and results in reasonably **higher cost and higher volume** per kW installed.
- Chargers **above 50kW** are more common to find in **city surrounding** or on the **highways**, where **transmission lines and transformers** are already present. Another possibility is to connect **energy storage systems** to enable extra power.
- On the other side, chargers **below 44kW** can be **directly connected to the grid**. Isolation between **grid and EV** is done through **high frequency transformer**. **More compact and cost advantageous** systems are achieved.
- **Charging time** will be of course **longer**, but this can be **compensated** by the **availability** of chargers nearby **home, office, shopping malls, etc.**




Source: ETH Zurich, modified

- Electro-vehicle (EV) Charger Introduction
- **Main Concept and Topologies**
- Practical Example
- Available Development Tools
- Q&A Session

# DC Chargers <50kW

## System Concept



3-ph Outlet

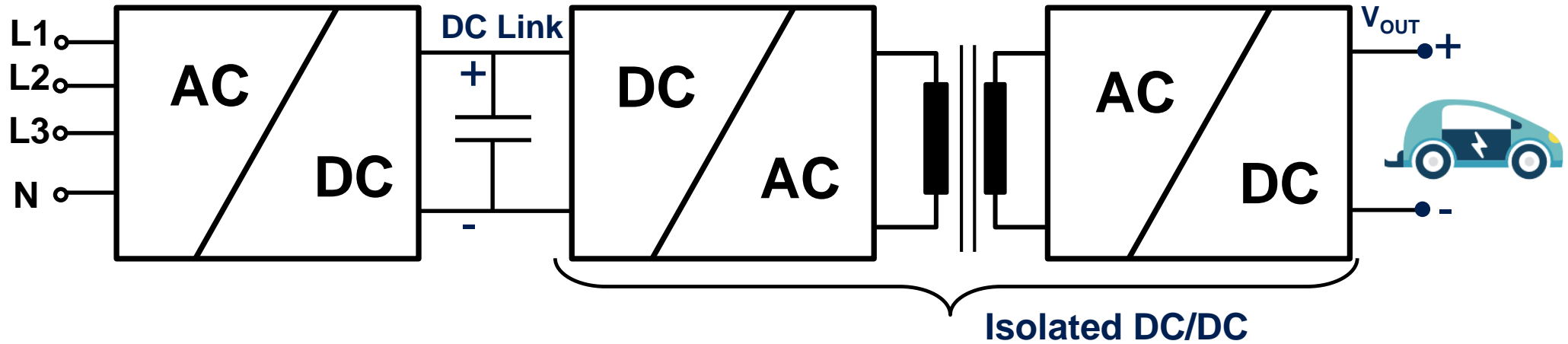


Parameter	Value
Input voltage	$L_x-L_y \rightarrow 400 \text{ V (RMS)}$ $L_x-N \rightarrow 230 \text{ V}_{AC}$
Link Voltage	400..1000 V
Nominal Power	11..44 kW
Output Voltage	200..500 $V_{DC}^*$

\*according to CharIn



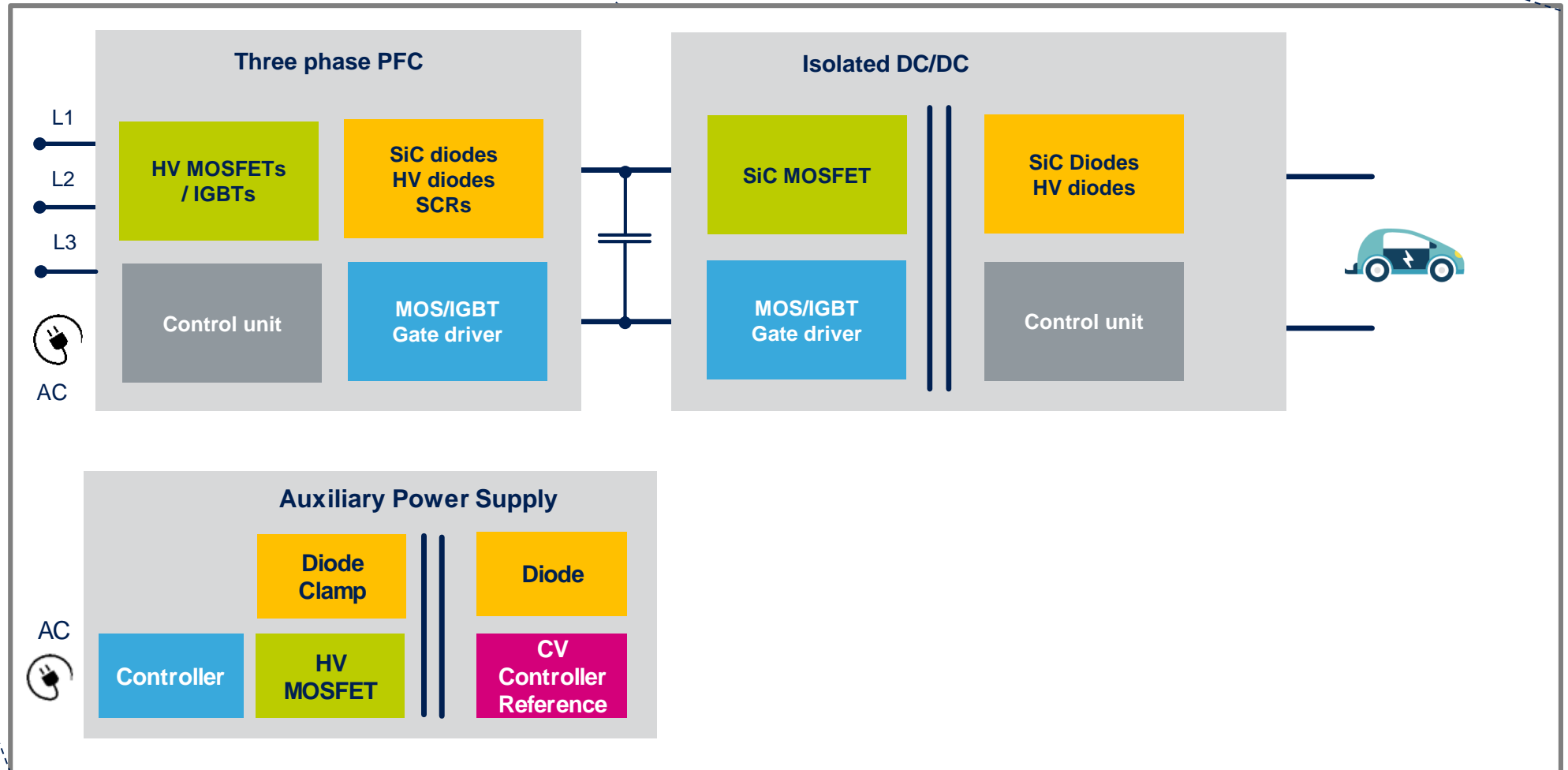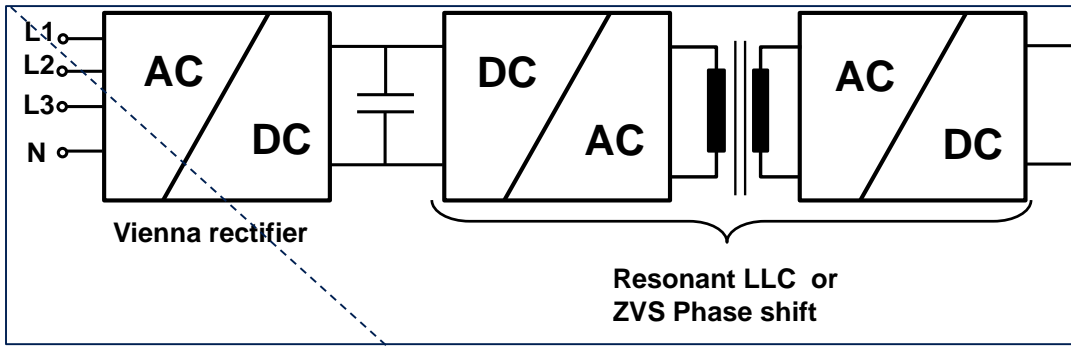


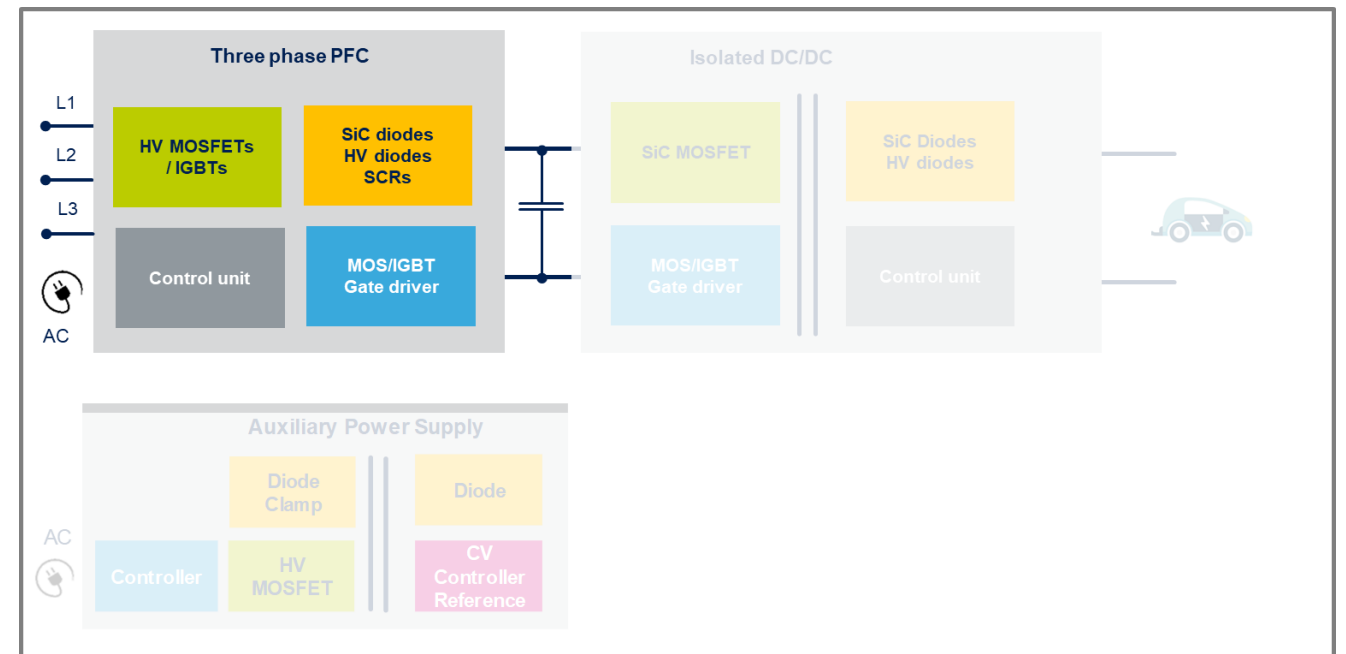- Electro-vehicle (EV) Charger Introduction
- Main Concept and Topologies
  - AC/DC Stage
  - DC/DC Stage
  - Bi-directional Charger
- Practical Example
- Available Development Tools
- Q&A Session



## 3x Independent 1-phase

Example: 3x PFC Booster

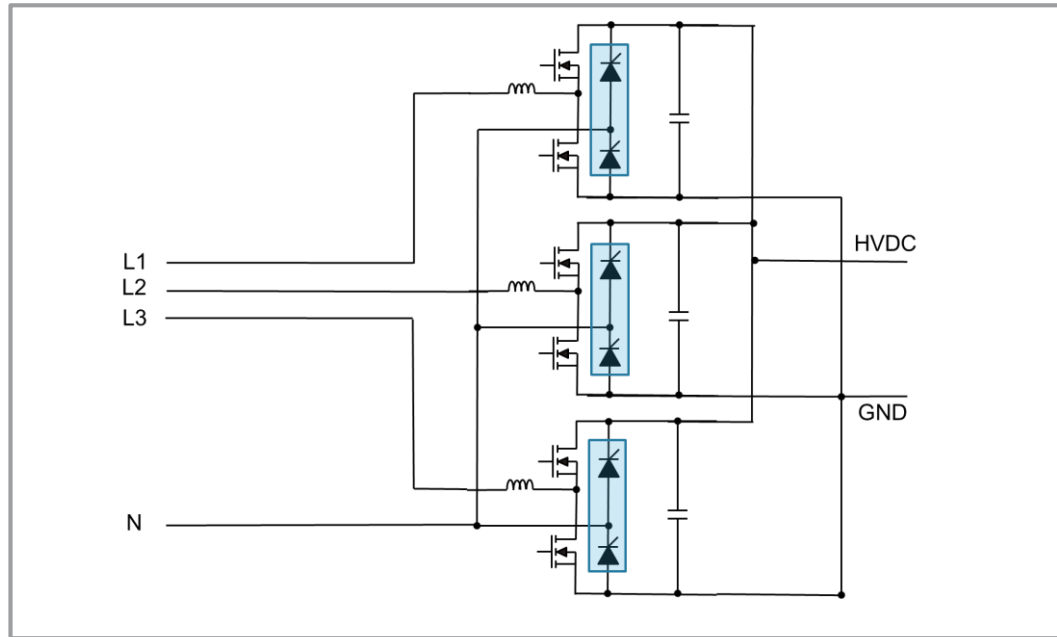

- + 4 devices / phase
- + Flexible grid configuration


- May need of 1200V SiC switches\*

\* In order to accomplish battery voltage requirements.



## 3-Level 3-Phase

Example: Mod. Vienna Type 1


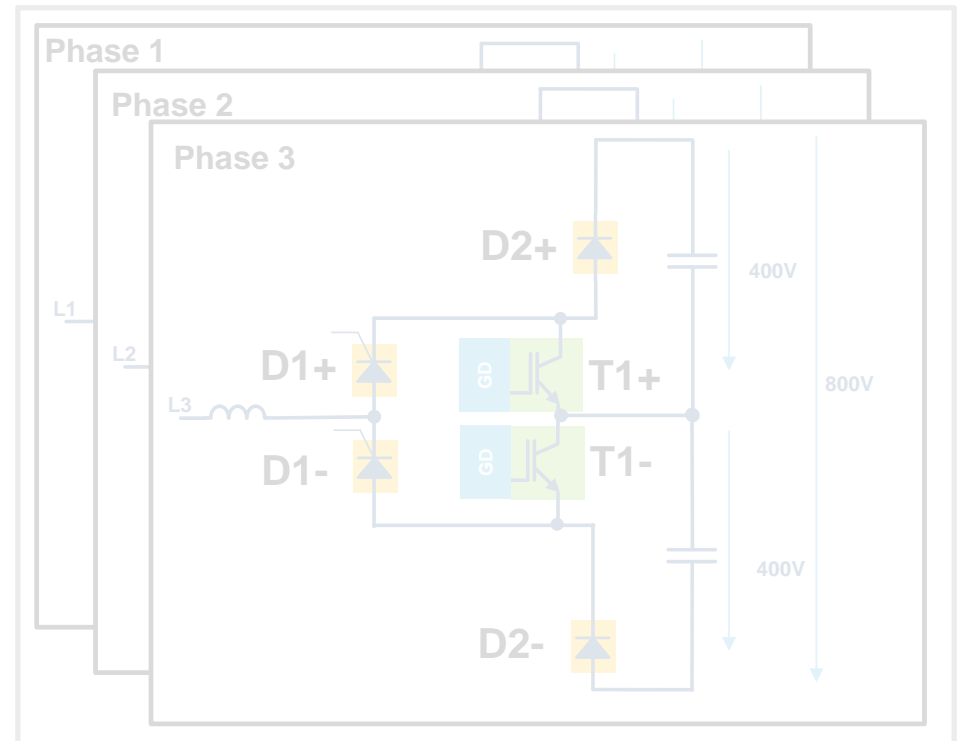


+ 650V Si Switches.

- 6 devices / phase.

# 3x 1-phase Topologies

## Standard PFC

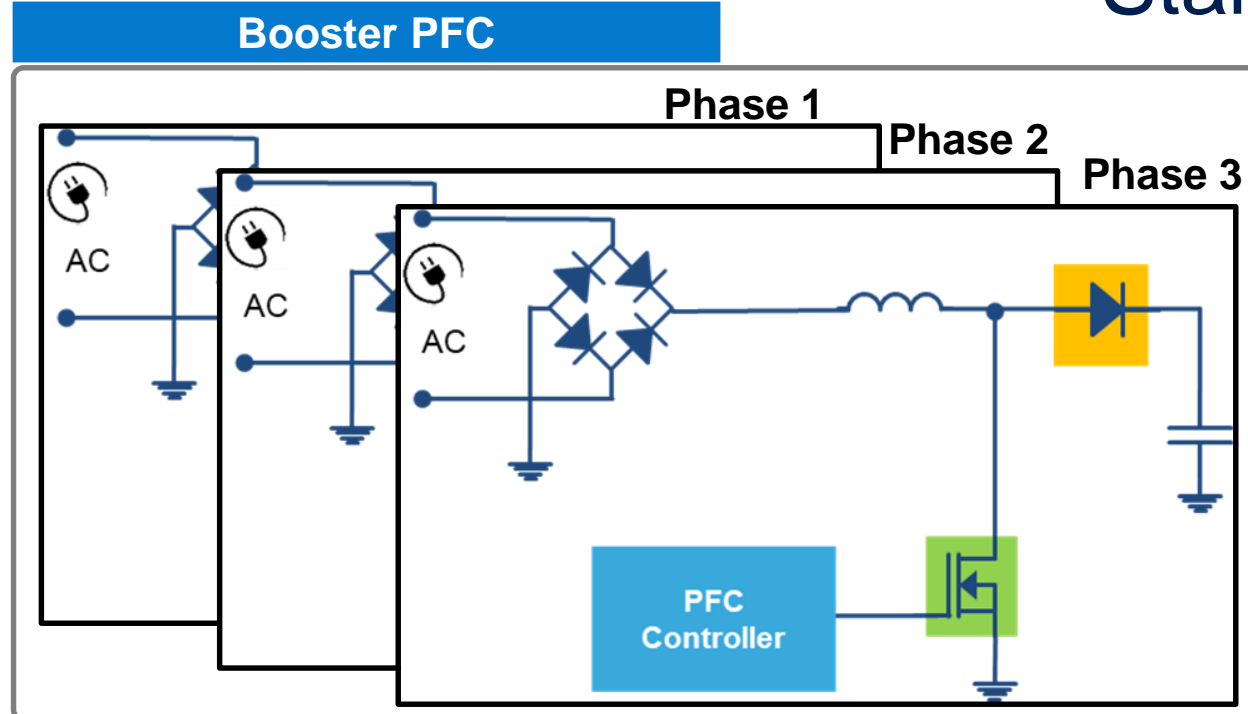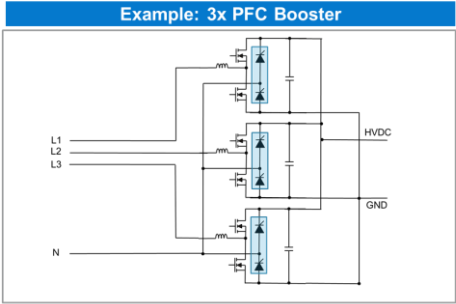


Required Semiconductor	ST Solution
Rectifier	STBRxx12W
SCR	TNxx50H-12WY
1200V SiC MOS	SCTxxN120
1200V SiC Diodes	STPSCxxH12C
Isolated driver	STGAP2S
Control	STM32 (Digital) STNRGPF0x (Mixed mode)

xx → Current class  
x → family name


Product page list in Slide 31

# 3x 1-phase Topologies

## Bridge-less Topologies

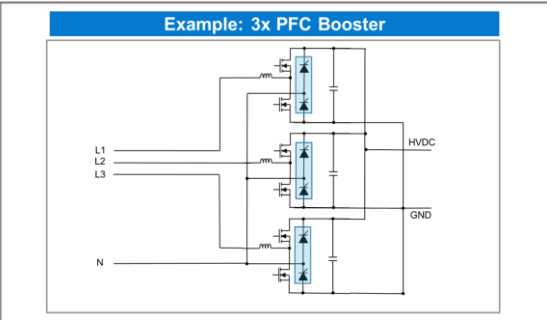


Var. 1 – Cost – Diode Leg

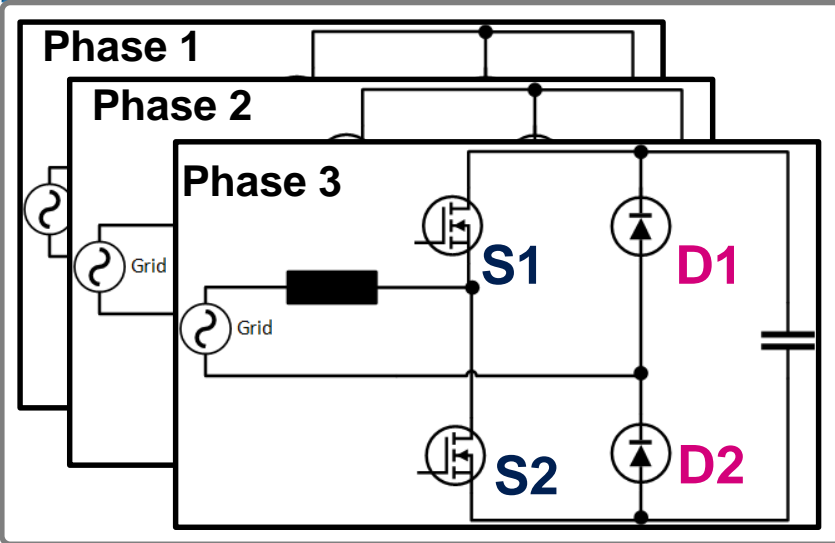


Device	Technology	ST Proposal
S1/S2	1200V SiC MOS	SCTxxN120
D1/D2	1200V Rectifier	STBRxx12W
	Driver	STGAP2S/D
	Control	STM32

Var. 2 – Performance – SiC MOS Leg

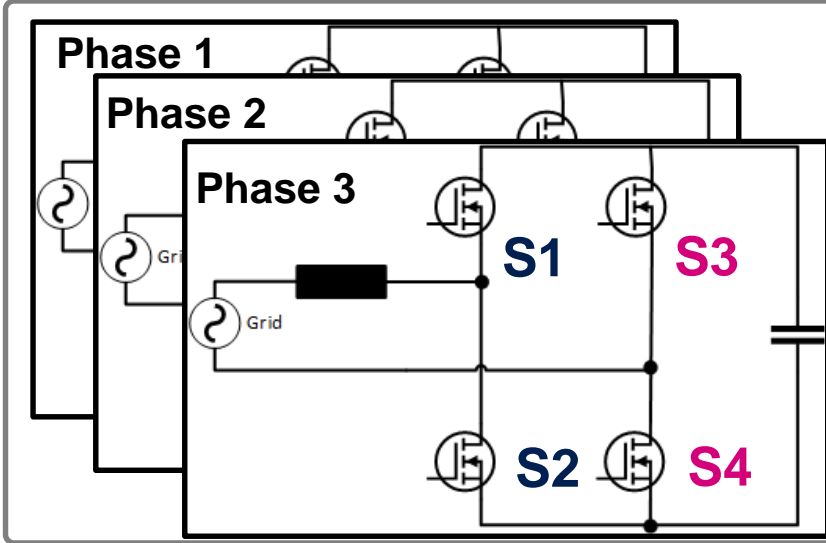

Device	Technology	ST Proposal
S1/S2	1200V SiC MOS	SCTWxxN120
S3/S4	1200V SiC MOS	SCTxxN120
	Driver	STGAP2S/D
	Control	STM32


Var. 3 – Relay-less – SCR Leg

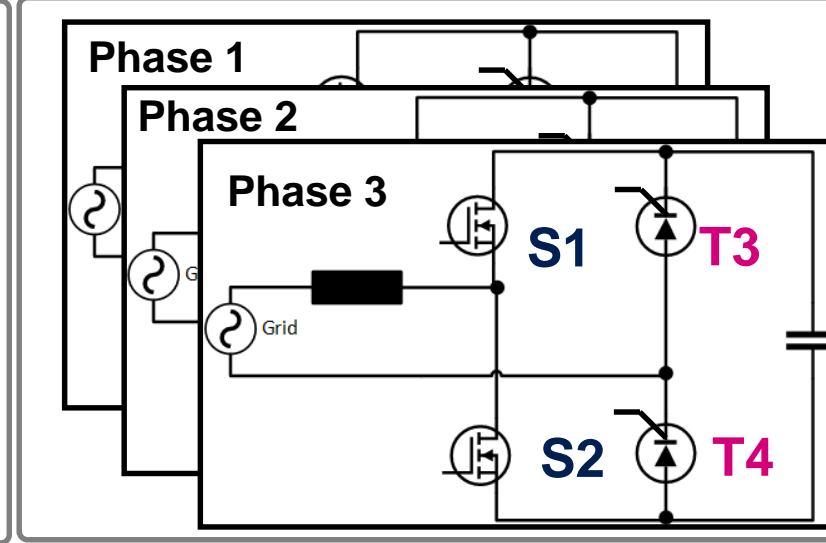

Device	Technology	ST Proposal
S1/S2	1200V SiC MOS	SCTxxN120
T3/T4	1200V SCR	TNxx50-12PI
	Driver	STGAP2S/D
	Control	STM32

## 3x Independent 1-phase

Example: 3x PFC Booster

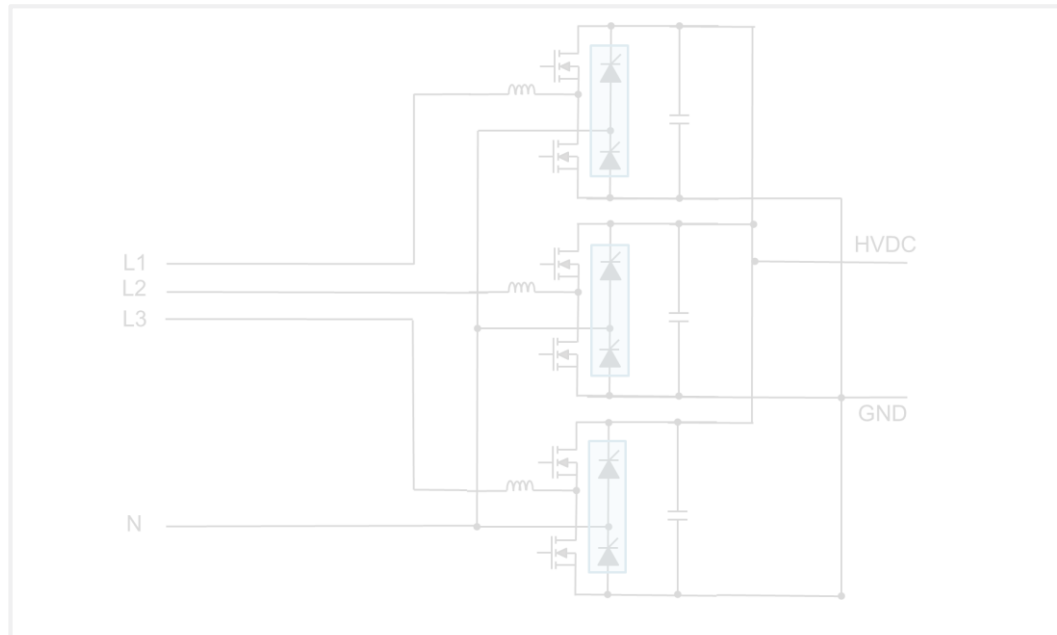

- + 4 devices / phase
- + Flexible grid configuration


- May need of 1200V SiC switches\*

\* In order to accomplish battery voltage requirements.




## 3-Level 3-Phase

Example: Mod. Vienna Type 1

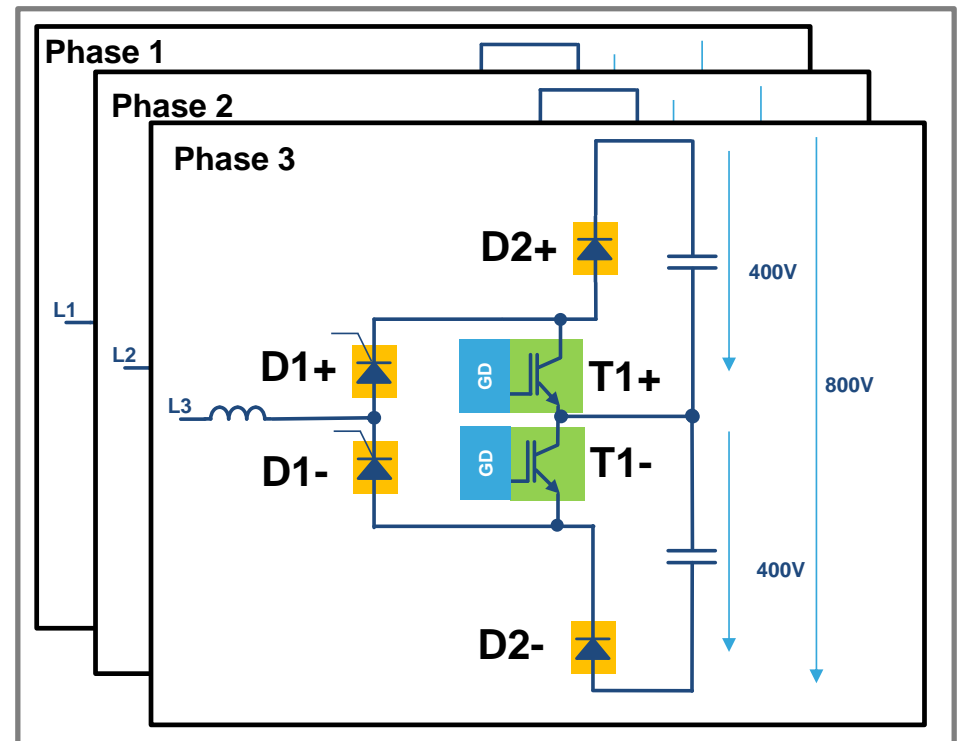


+ 650V Si Switches.

- 6 devices / phase.

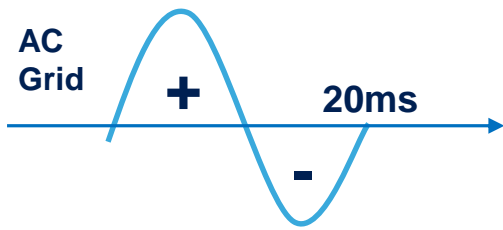

# Modified Vienna Rectifier Topology Comparison


**Mod. Vienna Type 1**

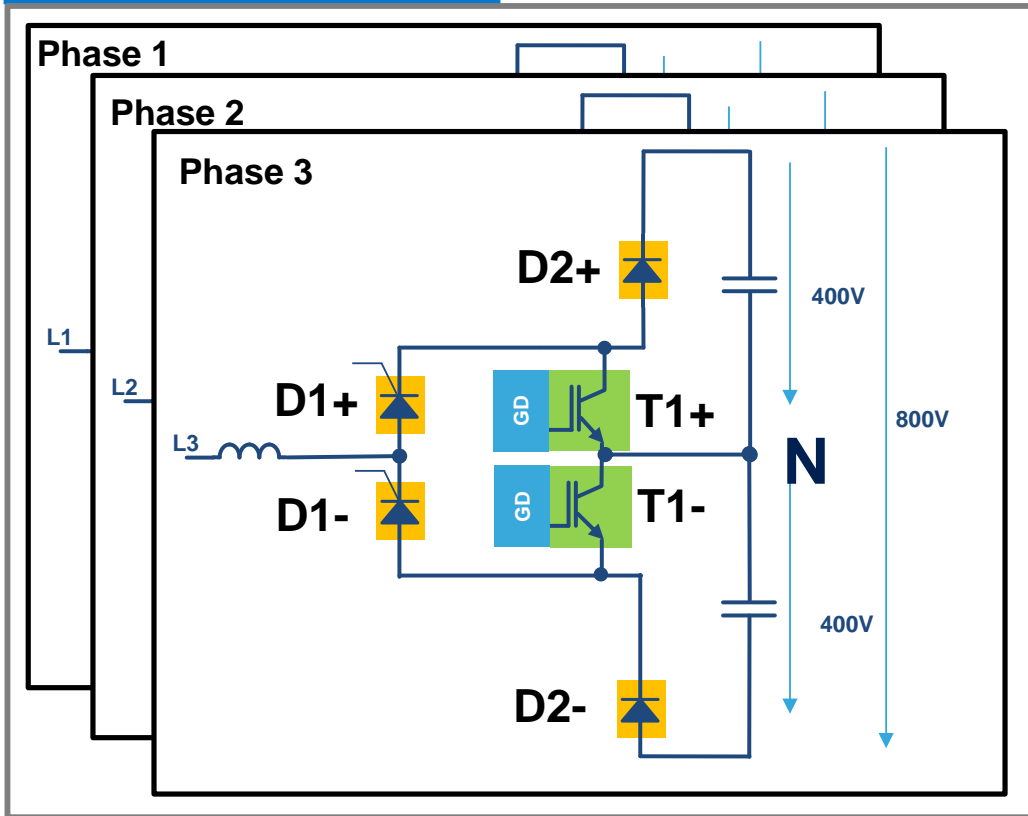

+ All 650V rated devices!  
→ lower cost

- 2 devices in the main current path (D1&D2)  
→ lower efficiency

**Mod. Vienna Type 2**

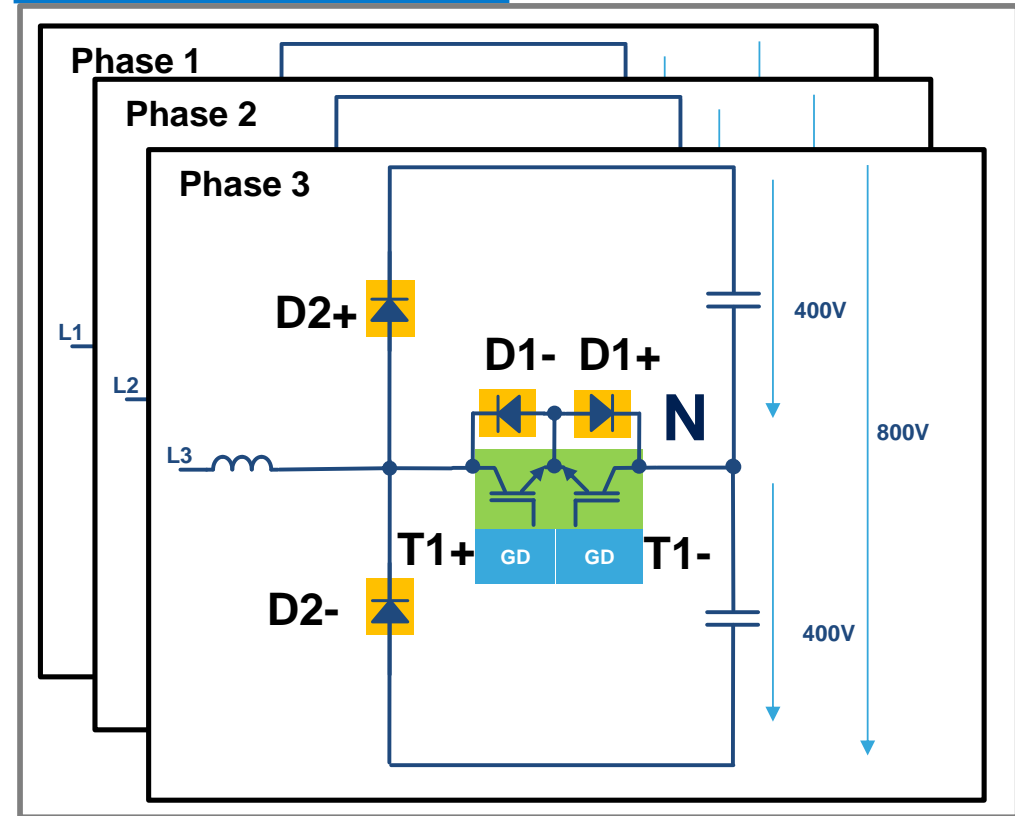


+ 1 device in the main current path (D2)  
→ Higher efficiency

- Need 1200V diodes (D2), typically SiC.  
→ Higher cost


# Topology Comparison

## Efficiency Comparison @ $P_{out}=20$ kW

Vienna rectifier Type 1

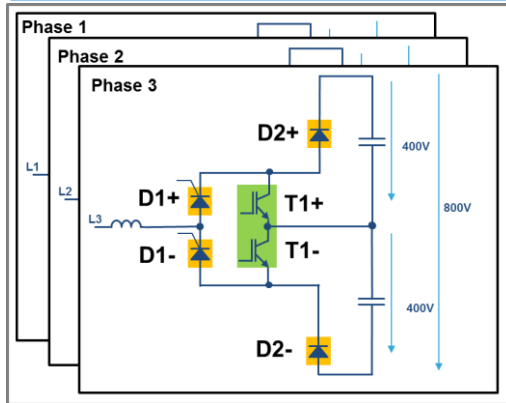



Vienna rectifier Type 2

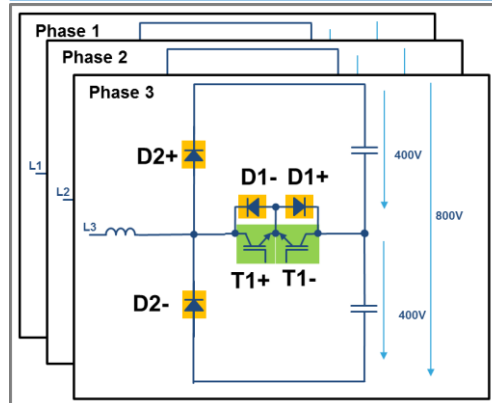

A → Eff. of IGBT: -0.3% than SJ/SiC MOS


B → Eff. of Type 1: -0.3% than Type 2

C → >50 kHz: SiC +0.1%..0.2% than SJ MOS

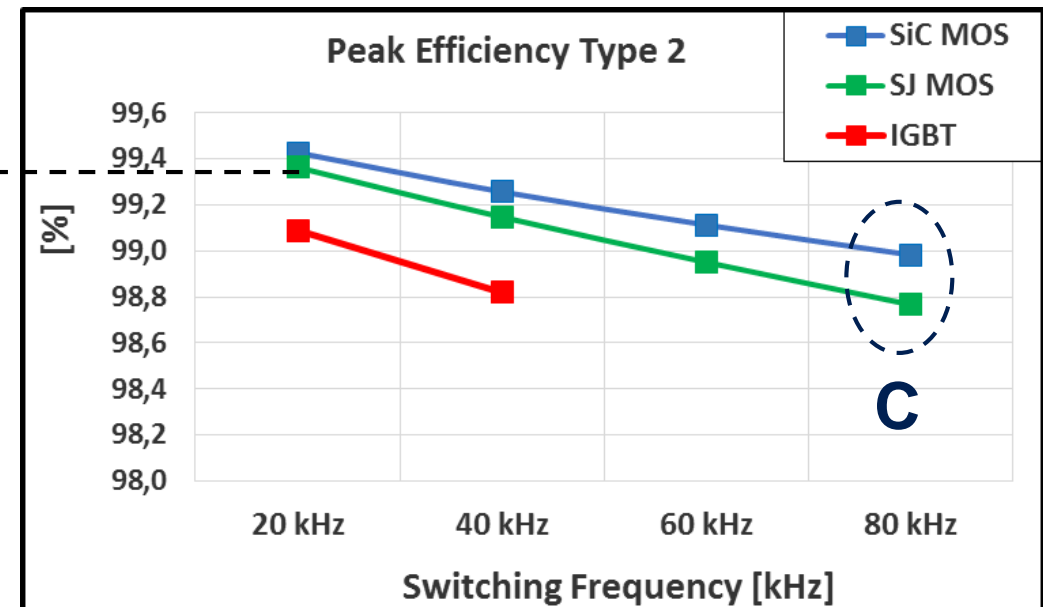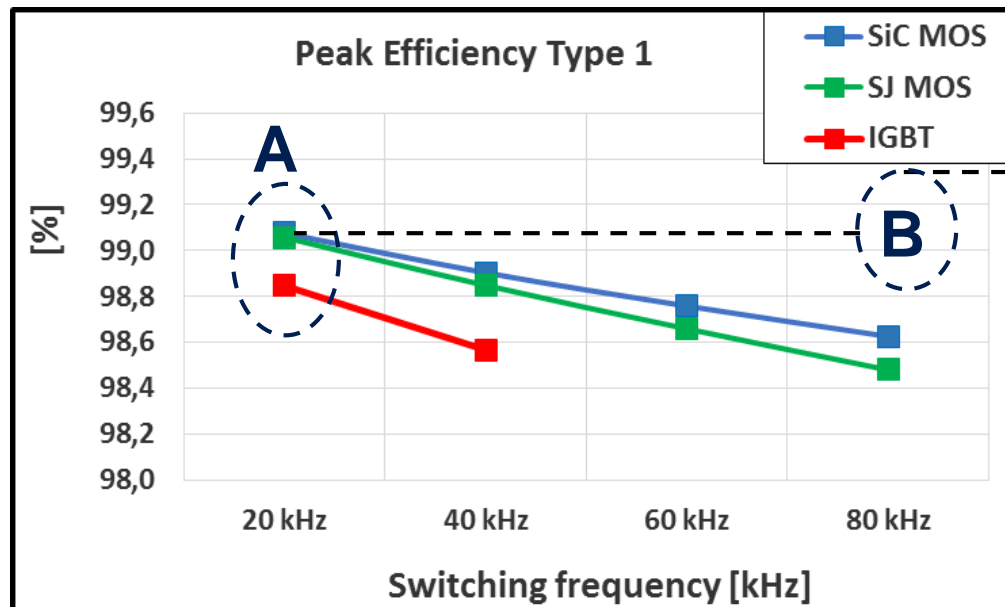


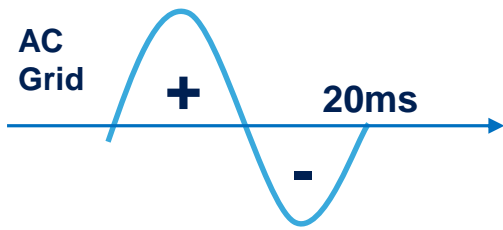
Simulated efficiency @  $T_j = 125^\circ\text{C}$ , considering only semiconductor losses.





# Modified Vienna Rectifier

## Device Proposal

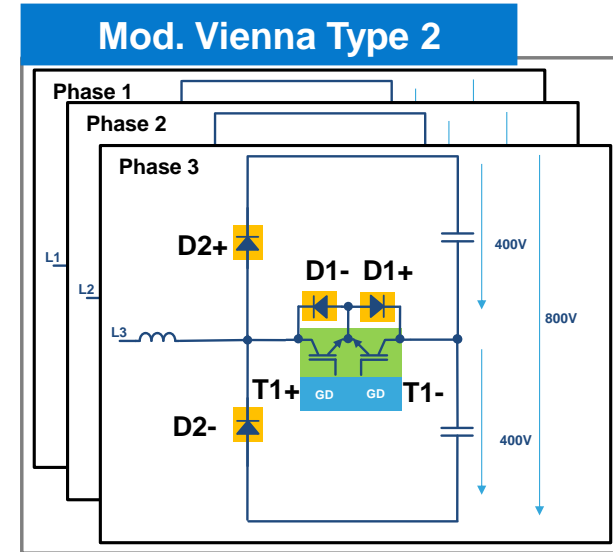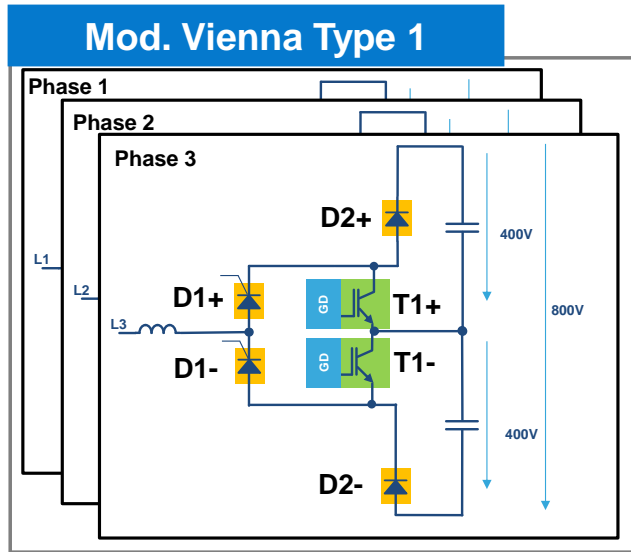


	Required Semiconductor	ST Solution
D1	Rectifier SCR	STBRxx12W TNxx50H-12WY
T1	650V IGBT 650V SJ MOS 650V SiC MOS	STGWaxxH65DFB2 STWxxN65M5 SCTWxxN65G2V
D2	600V FRD 650V SiC Diodes	STTHxxRQ06 STPSCxx065C
GD	Isolated driver	STGAP2S
	Control	STM32 (Digital) STNRGPF0x (Mixed mode)

	Required Semiconductor	ST Solution
T1/D1	650V IGBT 650V SJ MOS 650V SiC MOS	STGWaxxH65DFB2 STWxxN65M5 SCTWxxN65G2V
D2	1200V SiC Diode	STPSC40H12C
GD	Isolated driver	STGAP2S
	Control	STM32 (Digital) STNRGPF0x (Mixed mode)

xx → Current class  
x → family name


[Product page list in Slide 31](#)

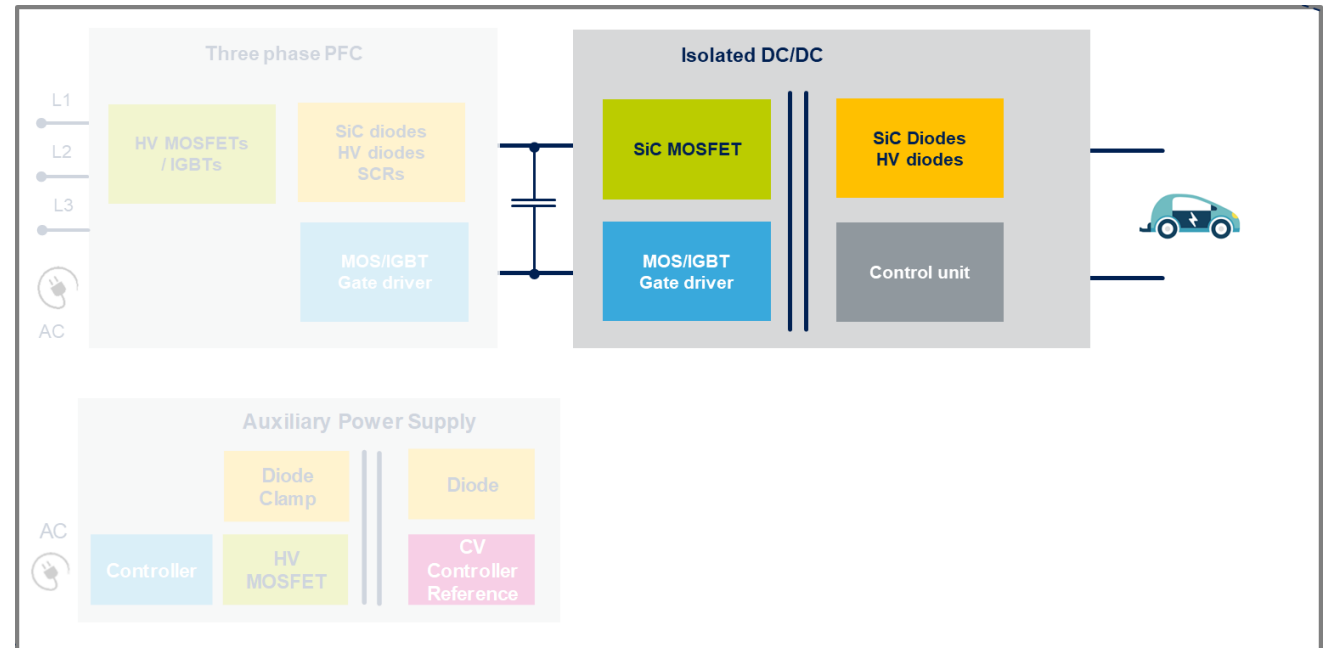- Electro-vehicle (EV) Charger Introduction
- Main Concept and Topologies
  - AC/DC Stage
  - DC/DC Stage
  - Bi-directional Charger
- Practical Example
- Available Development Tools
- Q&A Session



# DC/DC Stage Topologies

## LLC/ZVS

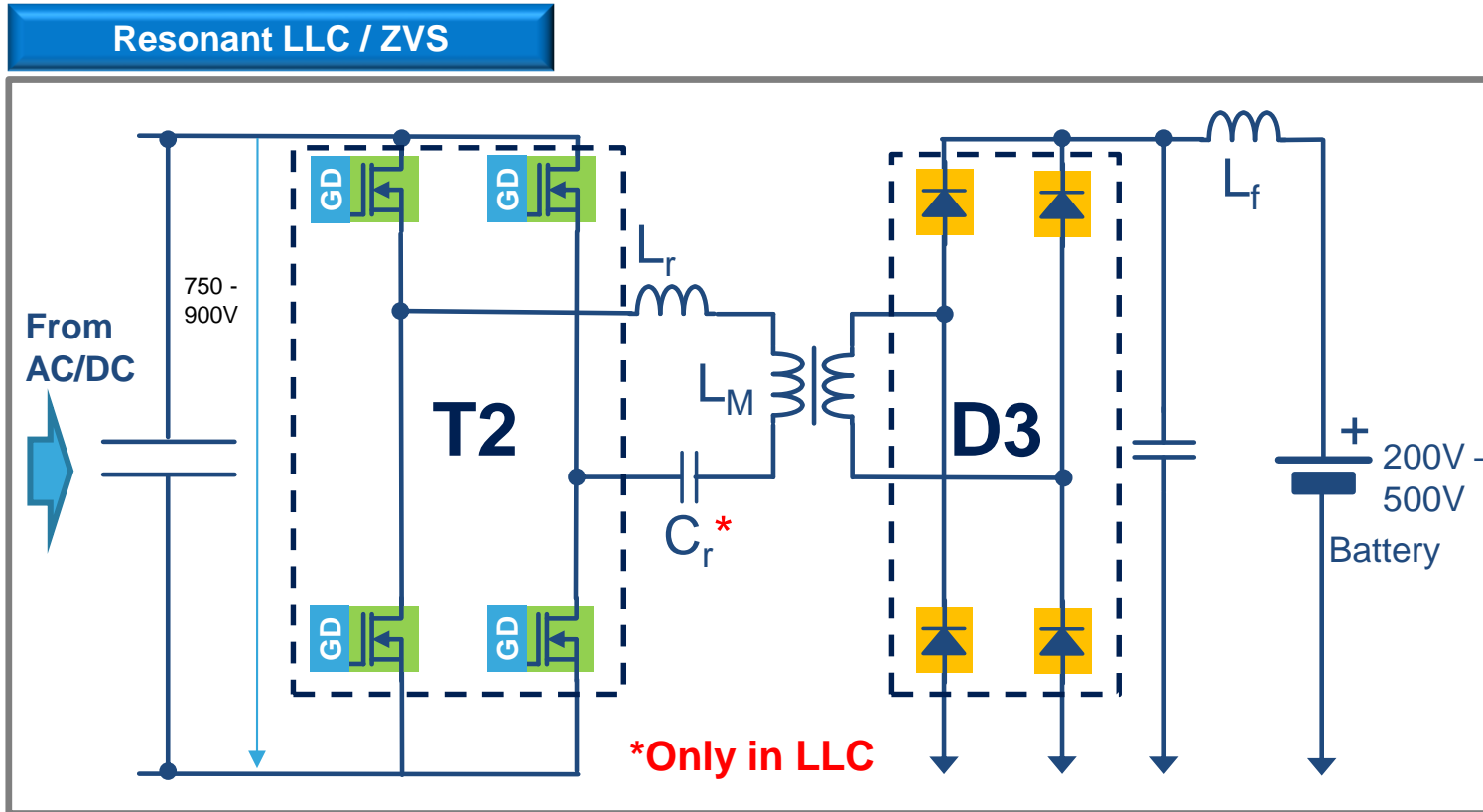


Device	Technology	ST Solution
T2	1200V SiC MOS	SCTxxN120
D3	600V FRD 1200V SiC Diodes	STTHxxRQ06 (LLC) STPSCxxH12C (ZVS)
GD	Isolated Driver	STGAP2S/D
Control	$\mu$ -Controller	STM32 (Digital)

xx → Current class

# DC/DC Stage Topologies



## Dual LLC/ZVS With Split DC Link

Resonant LLC/ZVS w/ Split DC Link

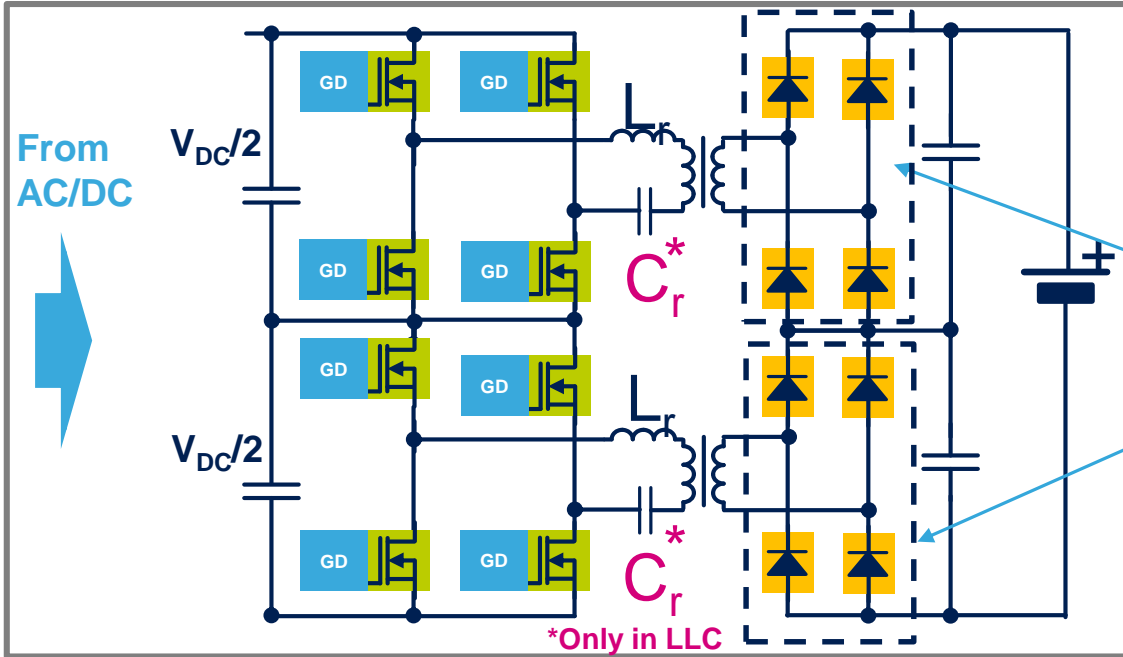


Can be connected in series or parallel, to accomplish high voltage batteries.

	Required Semiconductor	ST Solution
Primary switches	650V SJ MOS	STWxxN65DM6
Output Diodes	600V FRD 1200V SiC Diodes	STTHxxRQ06 (LLC) STPSCxxH12C (ZVS)
GD	Isolated driver	STGAP2S/D
Control	μ-Controller	STM32 (Digital)

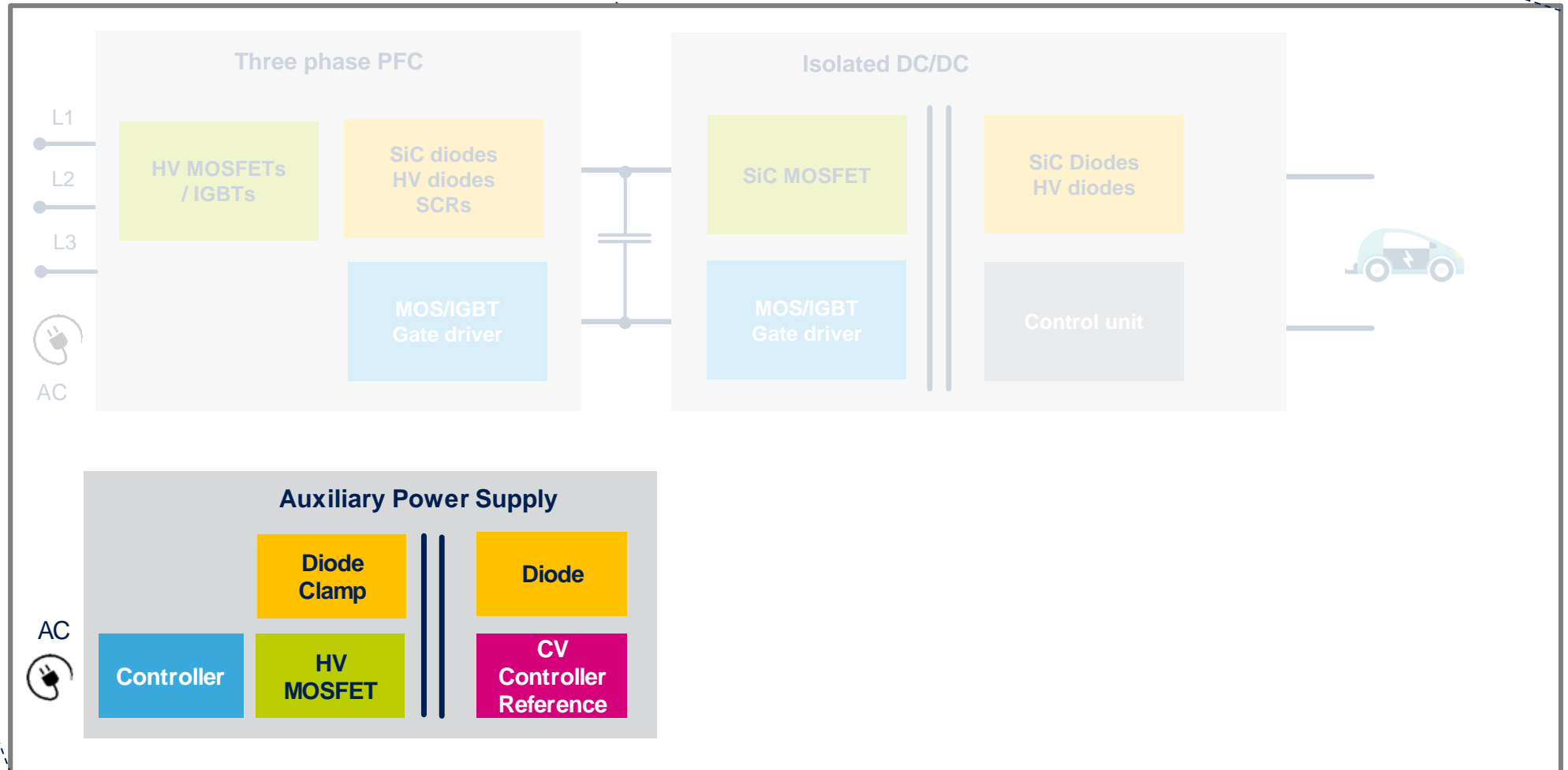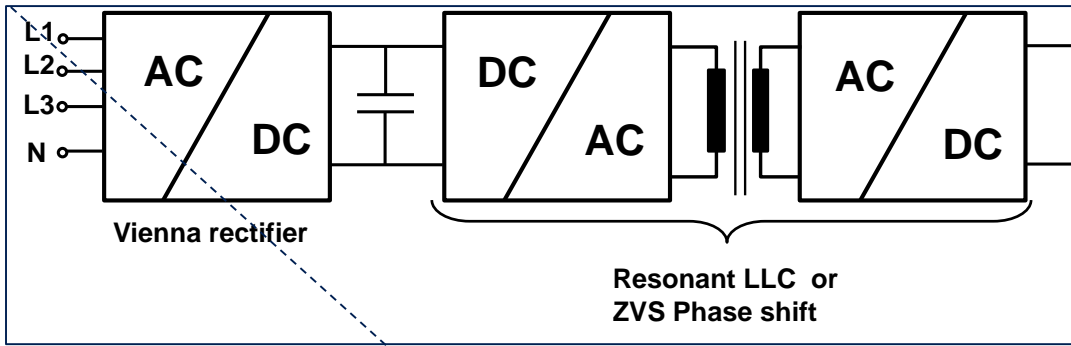

# Auxiliary Power Supply

## Circuit Topology and Proposed Devices

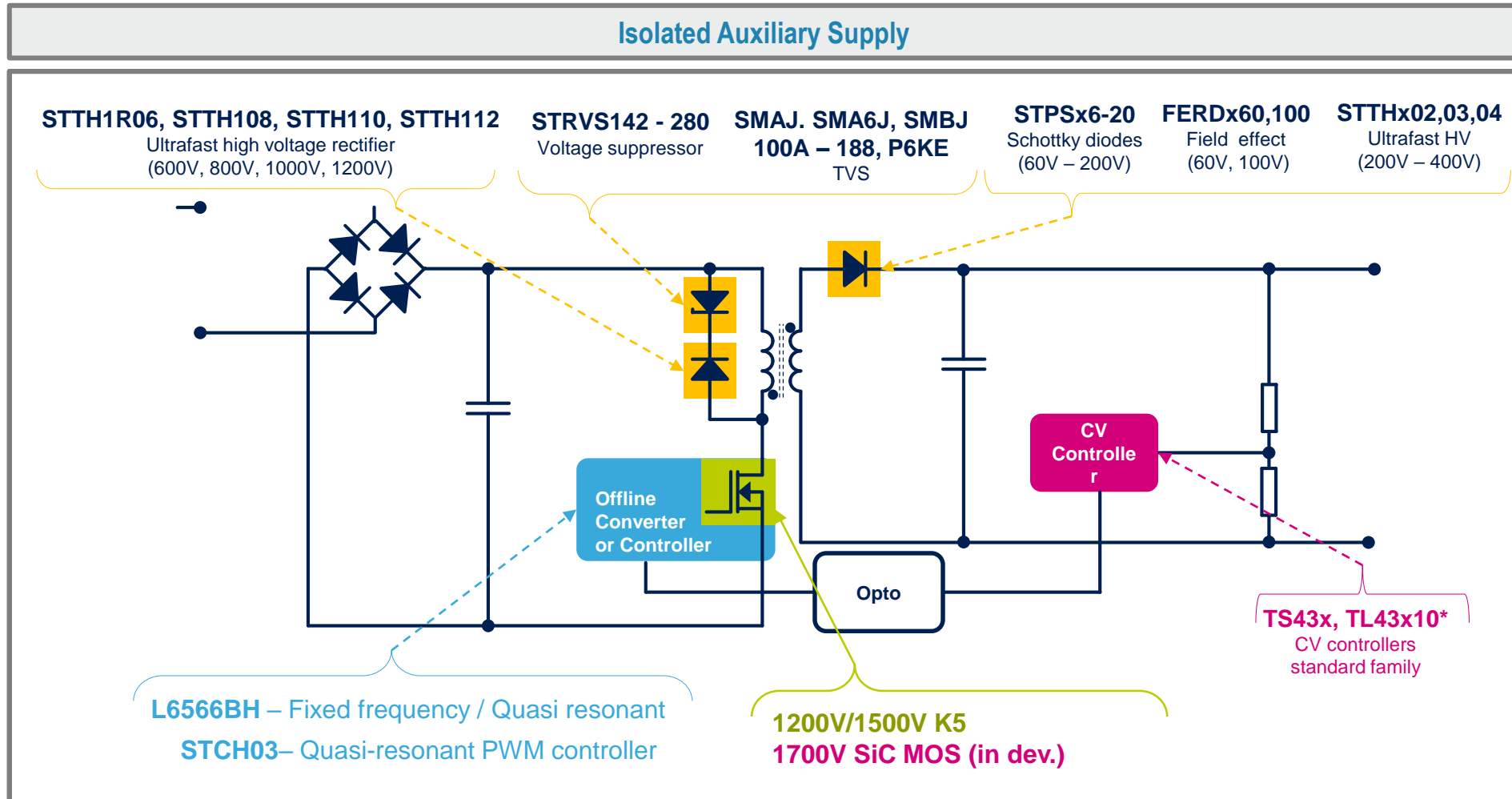


- Electro-vehicle (EV) Charger Introduction
- **Main Concept and Topologies**
  - AC/DC Stage
  - DC/DC Stage
  - **Bi-directional Charger**
- Practical Example
- Available Development Tools
- Q&A Session


# Bi-directional Charger

## AC/DC + DC/DC

### Bi-directional B6

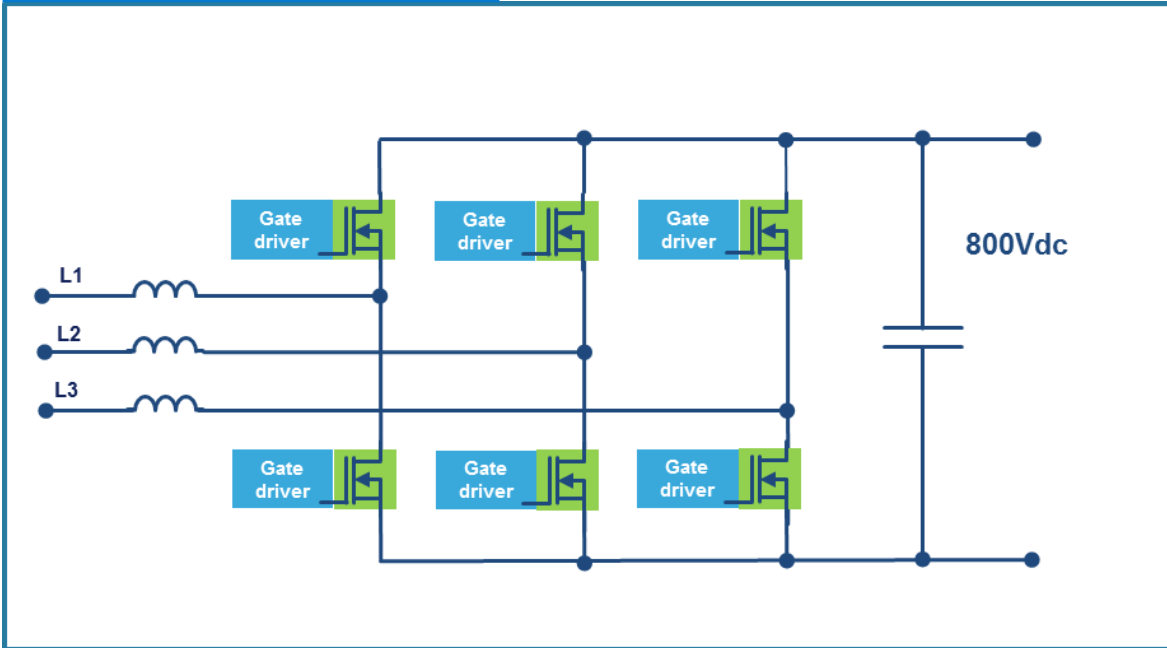
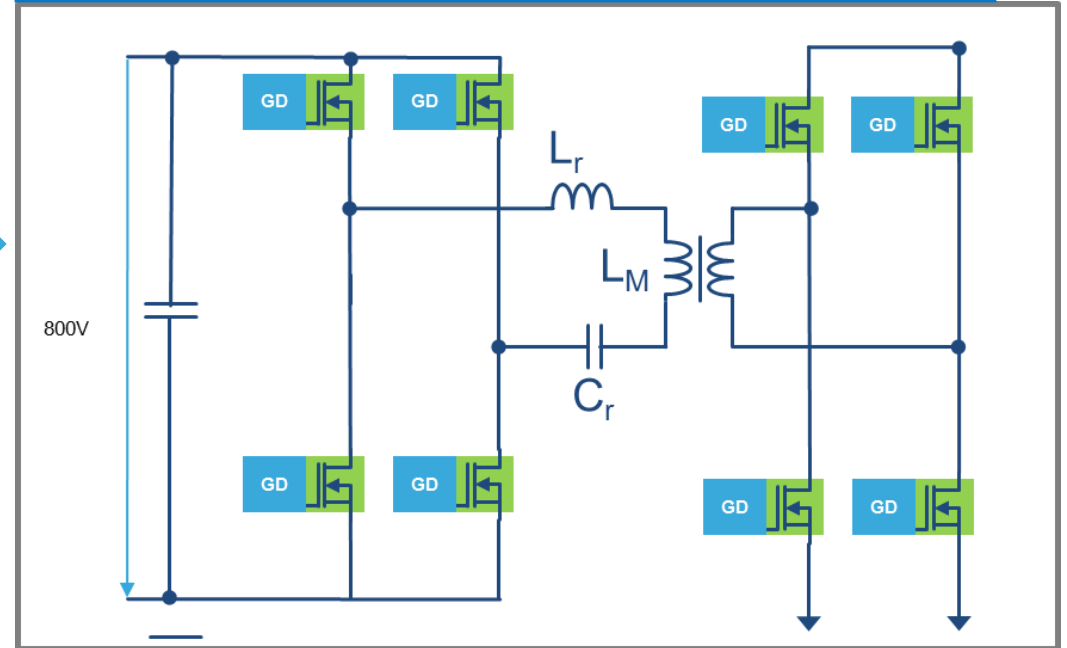
### Dual Active Bridge (DAB) / Bi-directional LLC



Stage	Required Semiconductor	ST Solution
B6	1200V SiC MOS	SCTxxN120
LLC/ZVS	650V SiC MOS 1200V SiC MOS	SCTxxN65G2V [400V Batt.] SCTxxN120 [800V Batt.]
Both	Iso Gate Driver	STGAP2S/D
Control	μ-Controller	STM32



- Electro-vehicle (EV) Charger Introduction
- Main Concept and Topologies
- **Practical Example**
- Available Development Tools
- Q&A Session

# Application Example



## DC Chargers for Electrical Vehicles

Parameter	Symbol	Value
Input voltage	$V_{in}$	230V <sub>ac</sub> Ph-N 400V <sub>ac</sub> ph-ph
Max. Input Current	$I_{in,max}$	32A/ph
Max Power	$P_{in,max}$	7.36 kW/ph 22 kW total
DC Link Voltage	$V_{DC}$	400..1000Vdc
Output Voltage	$V_{out}$	200..500Vdc



Configuration	SiC MOSFET	$R_{ds,on,typ}$ @ $T_j=25^\circ\text{C}$	Package	Number in parallel
Conf. 1	SCT50N120	52 m $\Omega$ @ $V_{gs}=20\text{V}$	HiP247	2x
Conf. 2	SCTW70N120G2V-4	25 m $\Omega$ @ $V_{gs}=18\text{V}$	TO-247-4 (Kelvin Source)	1x

# Comparison on Device Level

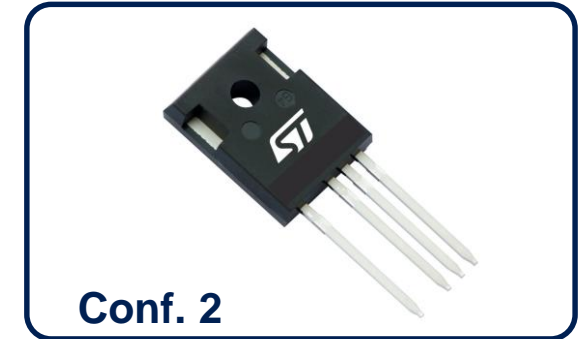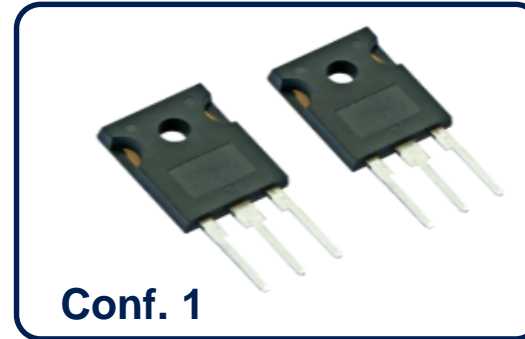



Parameter	Conditions	SCT50N120 (x2)	SCTW70N120G2V-4
$R_{ds,on}$	$V_{gs} = V_{g,op}, I_d = I_{d,nom}, T_j = 25^\circ C$	52 mΩ (26 mΩ)	25 mΩ
$R_{th,j-c}$	---	0.55 K/W (0.27 K/W)	0.45 K/W
$R_{th,c-h}$	---	~ 1 K/W (~0.5 K/W)	~ 1K/W

Dynamic Improvements must compensate thermal disadvantages of Conf. 2!

Parameter	Conditions	SCT50N120 (x2)	SCTW70N120G2V-4
$C_{ISS}$	$V_{ds} = 800V, V_{gs} = 0, f = 1MHz$	1900 pF (3800 pF)	3500 pF
$C_{OSS}$		170 pF (340 pF)	180 pF
$C_{RSS}$		30 pF (60 pF)	30 pF

# Experimental Results

## Comparison Gen 1 Vs. Gen 2 SiC MOS

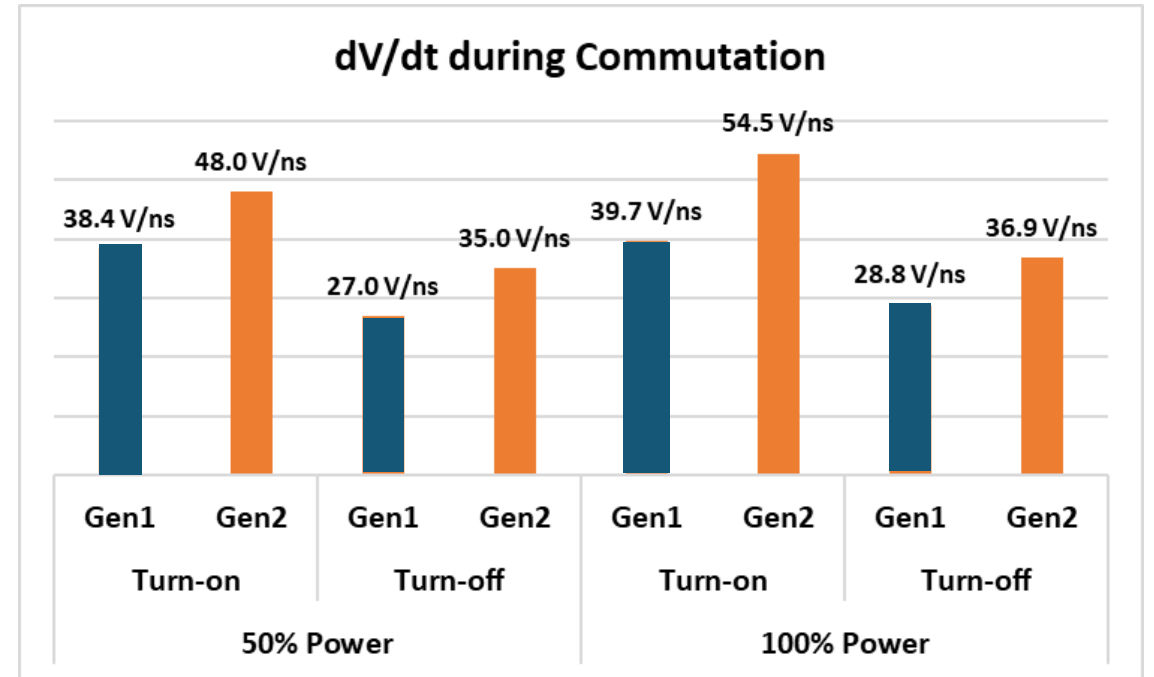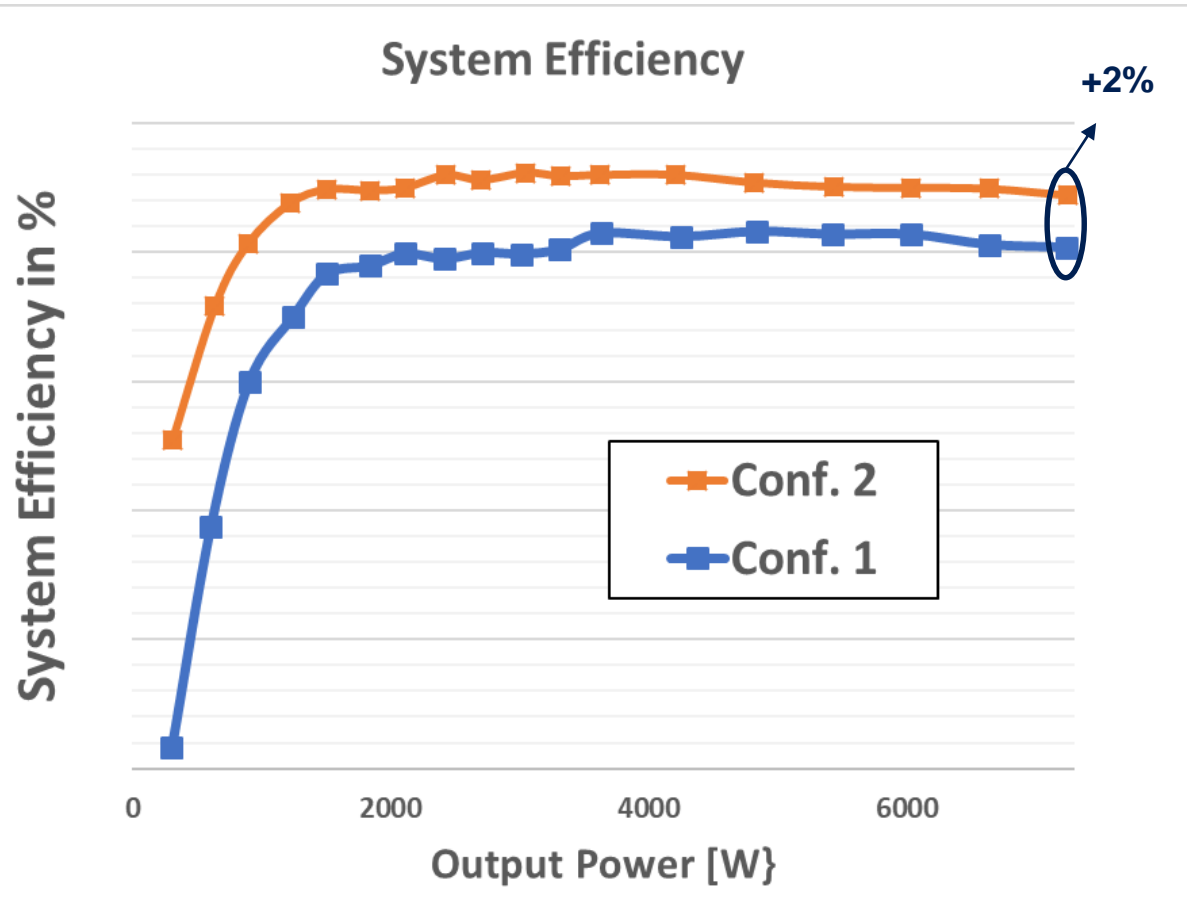

### Advantages on System Level


Parameter	Gain	Icon
Amount of switch devices	50% less	😊
Heat-sink size	40% smaller	😊
PCB area	26% smaller	😊
Commutation loop size	43% smaller	😊

- Electro-vehicle (EV) Charger Introduction
- Main Concept and Topologies
- Practical Example
- **Available Development Tools**
- Q&A Session
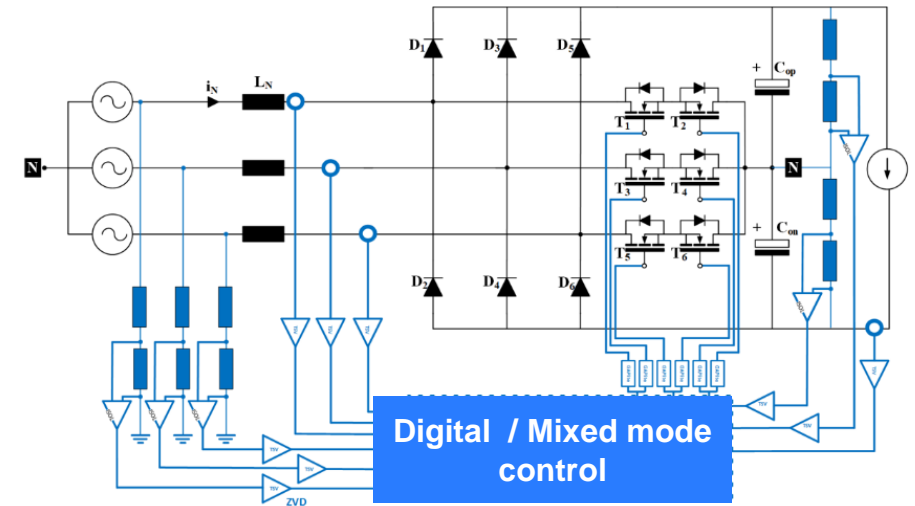
## 15 kW 3-ph PFC Converter

[Mod. Vienna Type 2]


- SCTW35N65G2V (SiC MOSFET);
- STPSC20H12 (SiC Diode);
- STNRGPF0x (controller, in development);
- STM32G474 (microcontroller)
- STGAP2S (Gate Driver).


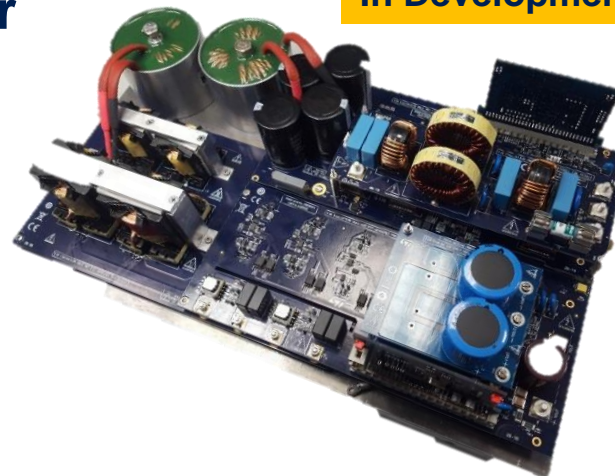
## 21 kW On Board Charger

[Totem pole + LLC Resonant]

- STTH30L06GY (rectifier);
- TN3050H-12GY (thyristor);
- STB47N60DM6AG (SJ MOS);
- STPSC20065GY (SiC Diode);
- SPC58NN84E7 ( $\mu$ -Controller);
- SCTH35N65G2V-7AG (SiC MOSFET).




In Development

## 100W AUX Power Supply

[Flyback]

Coming soon

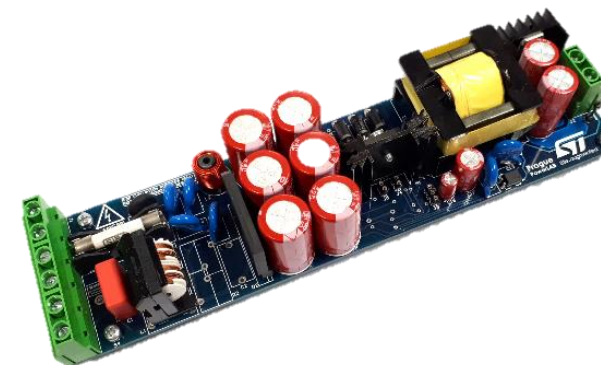


- L6566BH
- STW12N150K5
- STN1HMK60
- STPS10150
- TL431
- STTH112
- 1.5KE120A

- **Auxiliary Power Supply**
- [1200V/1500V Super Junction MOSFETs](#)
- [Protection Diodes](#)
- [Off-line controllers](#)
- [Power Schottky diodes](#)


- **Power Circuitry**
- [1200V & 650V Gen 2 SiC MOSFETs](#)
- [1200V & 650V SiC Diodes](#)
- [650V IGBTs](#)
- [600V FRDs](#)
- [650V Super Junction MOSFETs](#)
- [Isolated gate drivers](#)
- [STNRGPF01 Controller](#)
- [STM32 Microcontrollers](#)



# Application Tree – EV Charger

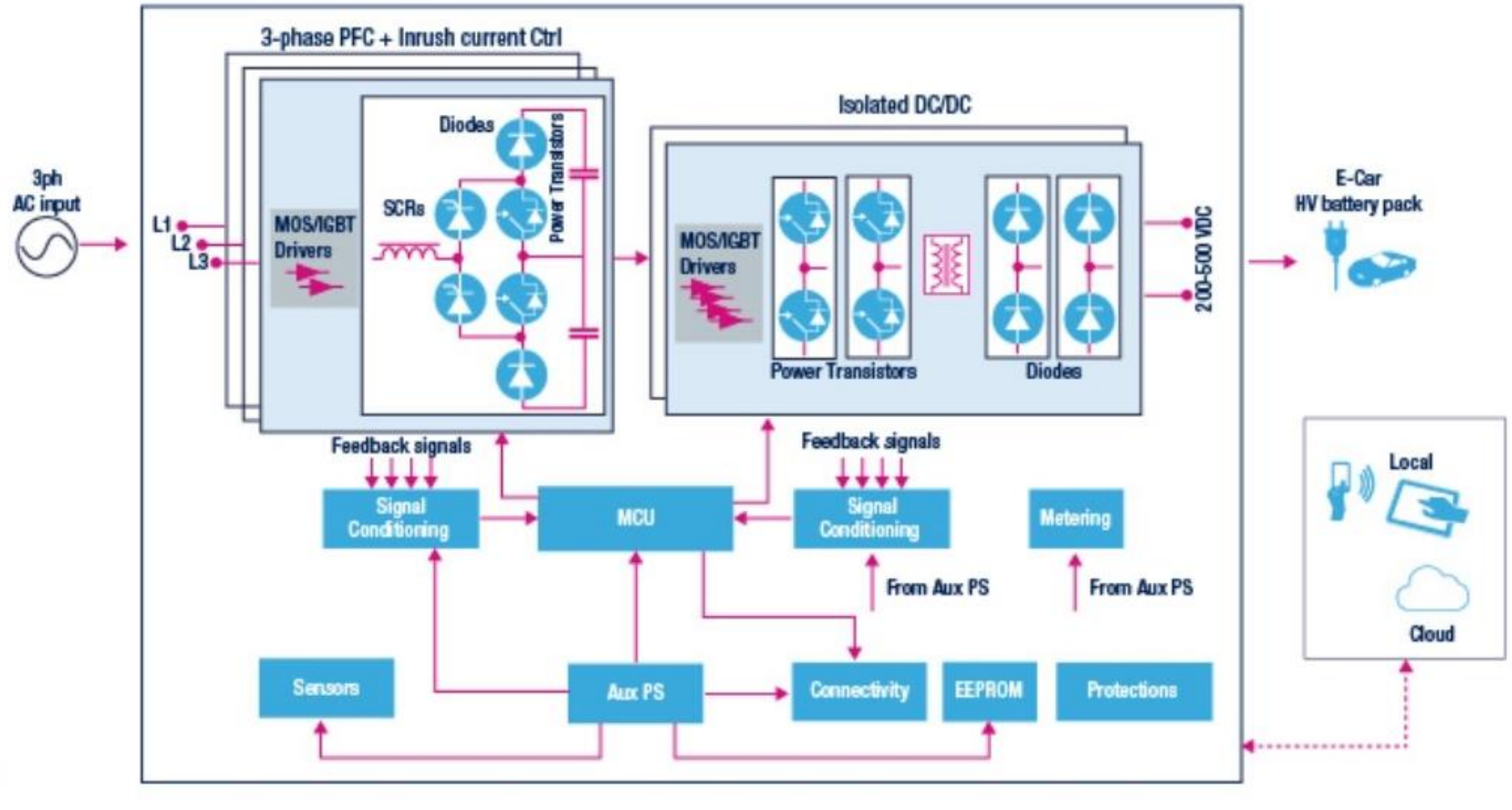



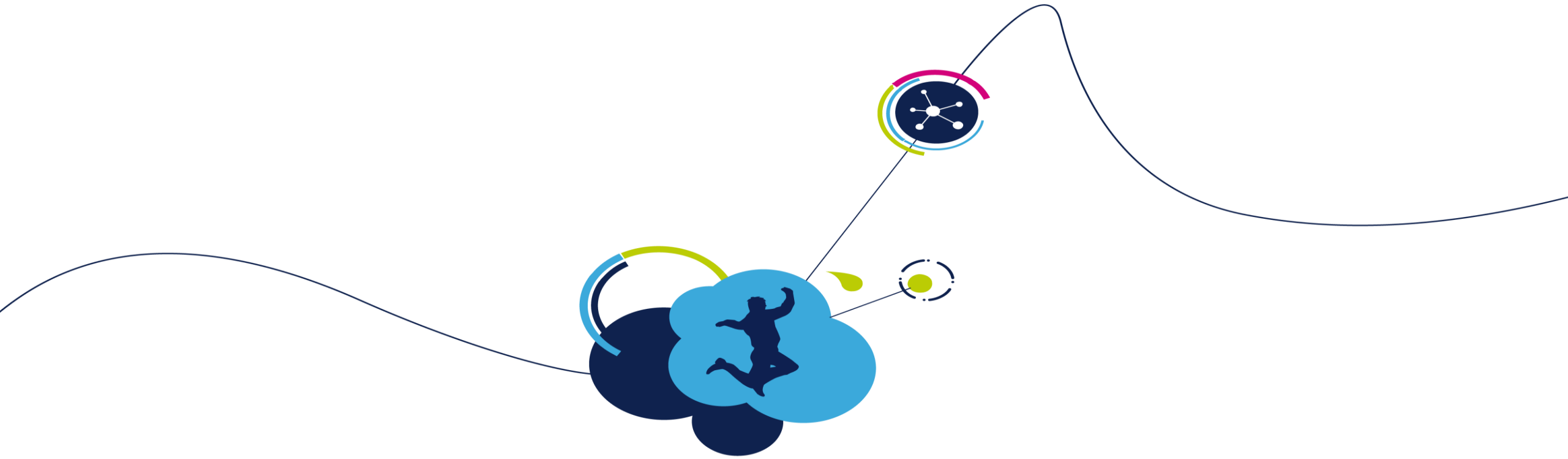

# Thank You for Your Attention!

Please Place Your Questions and Comments